

Rebuilding an Ex-RAF RECEIVER, Type 1155

By J. COOK

THE long suffering R1155 receiver has been adapted in many and various ways (vide articles in this magazine and others) but usually, one way or another, the performance and facilities fall short of those associated with the later types of communication receiver, as exemplified by the RCA-AR88, Hallicrafter SX28A or Eddystone 680, etc. Hence it is that, very often, the 'Ham' or short-wave enthusiast eventually scraps his R1155 and divests himself of some of his hard earned cash in purchasing one of these more advanced types of receiver.

In the author's case, however, it was decided that a really first-class communications receiver could be produced at a fraction of the cost using an R1155 as the basis. Moreover, it was considered uneconomic to utilise a separate domestic receiver for local 'quality' reception, so that the same equipment was required to fulfil this

The performance of the completed receiver is of a very high order combining, as it does, the high sensitivity of a communications receiver with the high quality reproduction of a TRF receiver feeding a push-pull Triode, Class 'A,' amplifier. Results on the higher frequencies with the converter unit, using double frequency changing, are exceptionally good also.

Construction

The first step is to strip the R1155 chassis mercilessly of all components except the handles, tuning gang with its associated dial and slow-motion assembly, wave-range switch, the three coil units for ranges 3, 4 and 5 mounted above the chassis, the 'Jones' socket nearest the side of the chassis, the three IF coil units and complete sub-chassis coil unit. The latter two items, whilst being retained as a whole, should be modified as described later. The tube holders


PRESENTING THE FIRST OF TWO INSTALMENTS OF THE WINNING ENTRY IN OUR RECENT RECEIVER CONTEST

function also — despite the difficulty that, normally, communications receivers are too complicated to be operated by non-technical members of the household.

It was thus that the receiver described in this article was evolved. The basis is an entirely re-built R1155 together with ancillary equipment comprising: converter for 5 to 10 metres, TRF unit with simplified control for medium-wave reception, TRF unit for television sound reception, dual speaker unit incorporating filter network and power pack unit supplying entire outfit. Whilst, perhaps, sounding ambitious the equipment can, nevertheless, be built up gradually. In any case, not all the above-mentioned facilities may be desired by the constructor. Economies can be effected, also, by replacing comparative luxuries such as the push-pull output stages by a single output tube, etc.

may also be retained but it may be found easier and advantageous to replace them with better quality components such as those of the 'Amphenol' variety, instead of the paxolin type employed.

It is necessary to cut a hole of the requisite diameter in the top right hand corner of the control panel to accommodate the 'S' meter. The meter illustrated is of $2\frac{1}{2}$ " diameter and, in this case, it was found best to cut the hole as near to the edges as possible in order to clear the adjacent controls. The antenna trimmer is mounted alongside the 'S' meter in the position where the tuning indicator was originally fitted and it is therefore necessary to fit a plate, similar to those already carrying the audio gain and BFO pitch controls, to carry this components. A plate, measuring 6" x 3" and drilled for an 1 1/8" octal tube holder, is required to be fitted

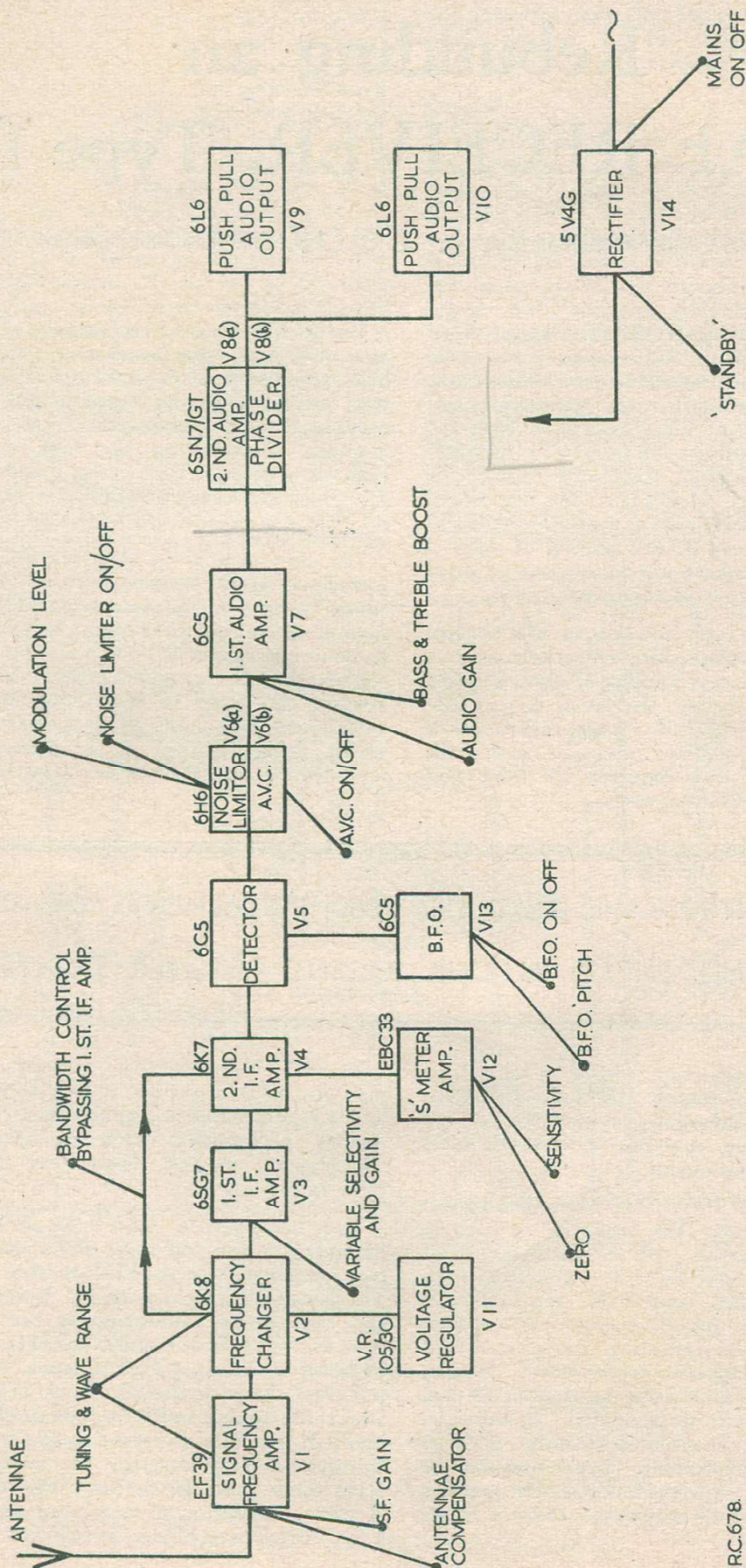

Block Diagram showing each stage with associated controls.

THE VALVE LINE-UP

Number on diagram	Function	Tube used (preferred type)	Alternative Type
V1	Signal Frequency Amplifier ✓	EF39	6K7
V2	Frequency-Changer ✓	6K8	ECH35
V3	1st. IF (Regenerative) Amp. ✓	6SG7	
V4	2nd. IF Amplifier ✓	6K7	EF39
V5	Infinite Impedance Detector	6C5	
V6(a), V6(b)	AVC and Noise-limiter	6H6 (metal)	
V7	1st. Audio Amplifier	6C5	6SJ7 (see remarks)
V8(a), V8(b)	2nd. Audio Amp. and Phase Divider	6SN7/GT	
V9, V10	Push-pull, Class 'A,' Triode connected amplifiers	Two 6L6 (metal)	Various
V11	Voltage Stabiliser	VR105/30	
V12	'S' Meter Amplifier	EBC33	6Q7/GT or metal
V13	Beat Frequency Oscillator	6C5	
V14	Rectifier	5V4/G	

to the chassis, below the 'S' meter and in line with the other two tube holders, to carry V8 and the output transformer. Another plate measuring 2 9/10" x 2 4/10" is fitted in place of the two 'Jones' sockets which have been removed to accommodate the two antenna input sockets and the two output jacks. Additional holes will be necessary to carry the selectivity, negative-feedback (if required), BFO on/off, HT on/off, noise-limiter bias, SF gain and 'S' meter zero controls. These modifications will be more clearly appreciated from Fig. 1. Dimensions are not indicated as they depend to a great extent on the size of the components used—small components are generally desirable in order to fit them in the available space. A small aluminium chassis, 2 4/10" x 5" x 1 1/4" is fitted above the receiver deck to house the beat frequency oscillator (in its original position) by means of angle brackets bolted to the existing holes.

It is a good plan to protect the tuning gang with a cover of some sort whilst the above modifications are being carried out in order to avoid the danger of filings lodging between the vanes—such an occurrence would be more than a nuisance! Finally, before the drill is laid aside, a word of warning. In order to avoid confusion between this receiver, when it is operating, and an electric toaster—it is both necessary and desirable to arrange for additional ventilation for the 13 tubes housed in such narrow confines. This can be accomplished easily by cutting a series of holes in two rows in the back and sides; a chassis cutter is a good tool for this purpose. At the same time, the fitment of rubber feet to the base of the cabinet will be found very useful to help clear the many cables under the cabinet, thus making a neat installation.

Before proceeding with the wiring side of the construction, it is assumed that the constructor will adhere to the good rules of radio; i.e., short

and direct wiring, substantial earthing, use of heavy gauge wire, etc. Further mention of these points will not, therefore, be made except where especial attention is necessary. It should be noted that neither side of the heater circuit is taken to chassis as a 3-volt potential will now exist between either of these points and chassis due to the centre-tapped transformer used. This arrangement reduces the chances of heater borne hum being introduced as, also, does twisting the heater wires together. These wires must be capable of carrying the load current without any drop as it must be borne in mind that up to 3 amps passes at some points.

Signal Frequency Amplifier and Frequency Changer

These two stages utilise EF39 and 6K8 tubes respectively, their bases being enclosed in the main coil switching unit. Two antenna input sockets are mounted on the front panel; one is provided for use with a long wire antenna whilst a co-axial socket is used for di-pole antenna or converter input. In the latter instance it is absolutely necessary for the input to be properly screened. A series capacitor is included in the antenna input and may be conveniently mounted outside the coil compartment.

The majority of the SF stage components are housed in the smaller of the two compartments and a number of modifications are necessary. The switch wafer, nearest the audio stages, which controls the primary of the input coil should be altered as follows:—

Upper series of contacts: The input from the antenna capacitor is connected to the key contact to feed coils on ranges 3, 4 and 5. Remaining wires are removed.

Lower series of contacts: The key contact is wired to chassis whilst remaining connections are unchanged.

The SFA coils for ranges 3, 4 and 5 are mounted


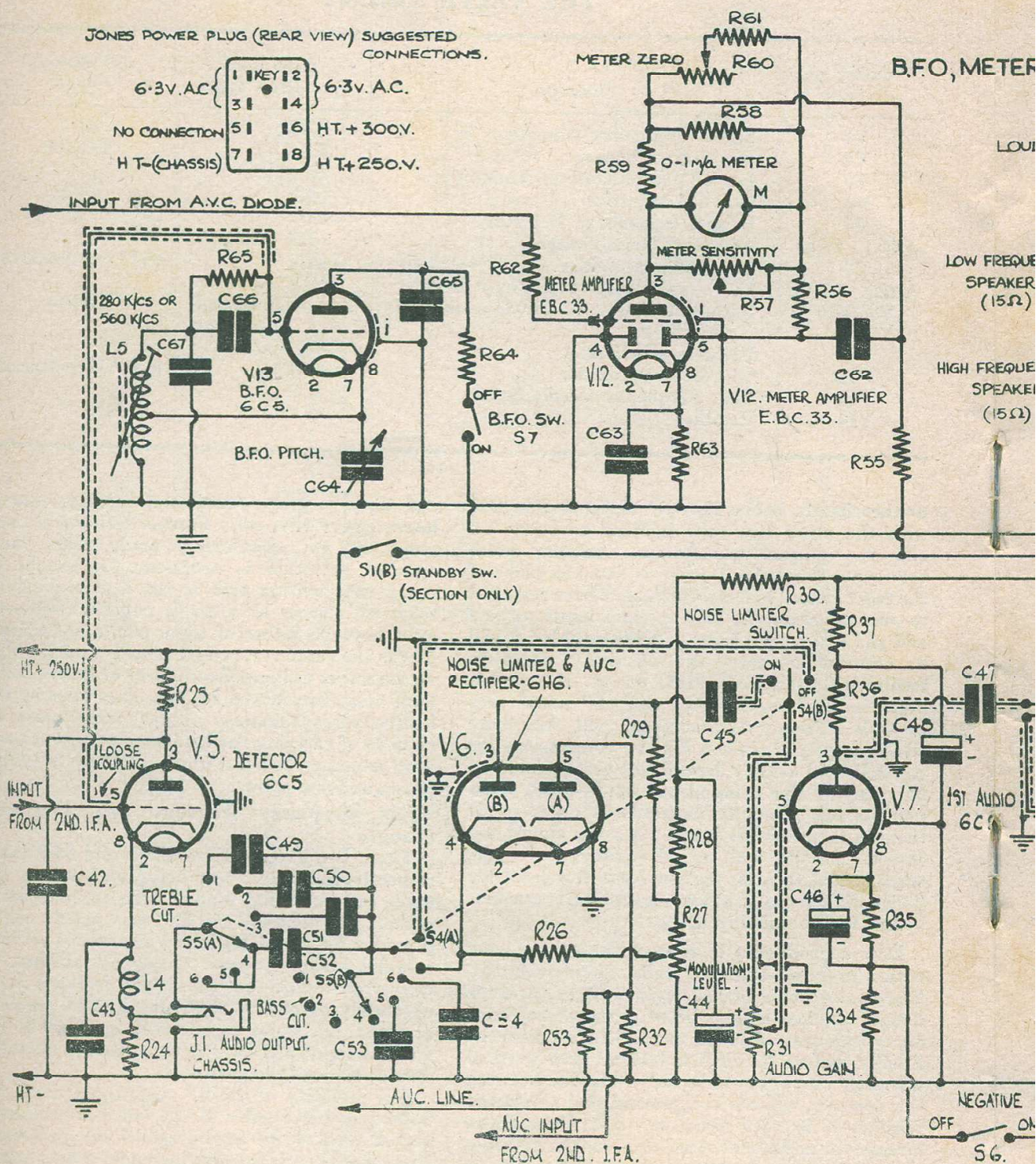
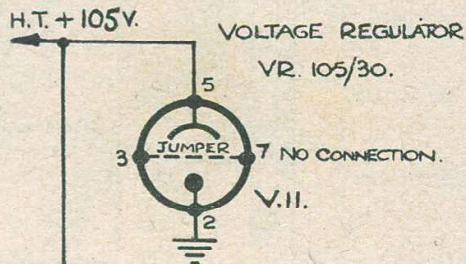


Fig. 2b. Circuit of the BFO, Meter Amplifier, Detector, Noise Limiter, Voltage Regulator, and Audio Stages of the Receiver. Component values are given on page 228. The circuit of the Signal Frequency Section is given on page 227.

TER AMPLIFIER, DETECTOR, NOISE LIMITER, VOLTAGE REGULATOR & AUDIO STAGES.


LOUDSPEAKER DIVIDING NETWORK

(CROSSOVER $f = 1000$ c/s.)

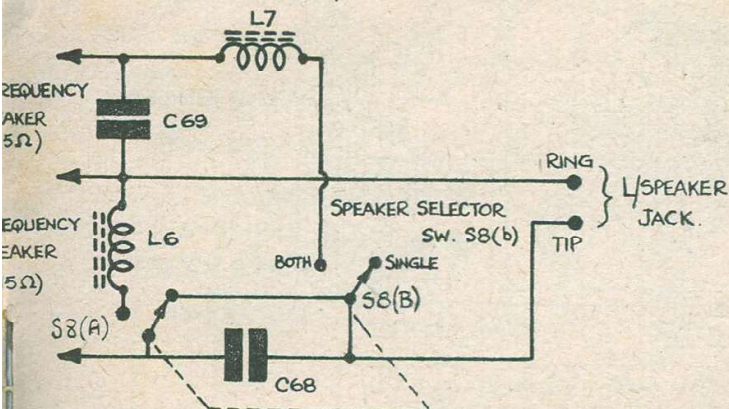


CONNECTIONS TO POWER PLUG.

HT + 250V. PIN 8
HT + 300V. PIN 6

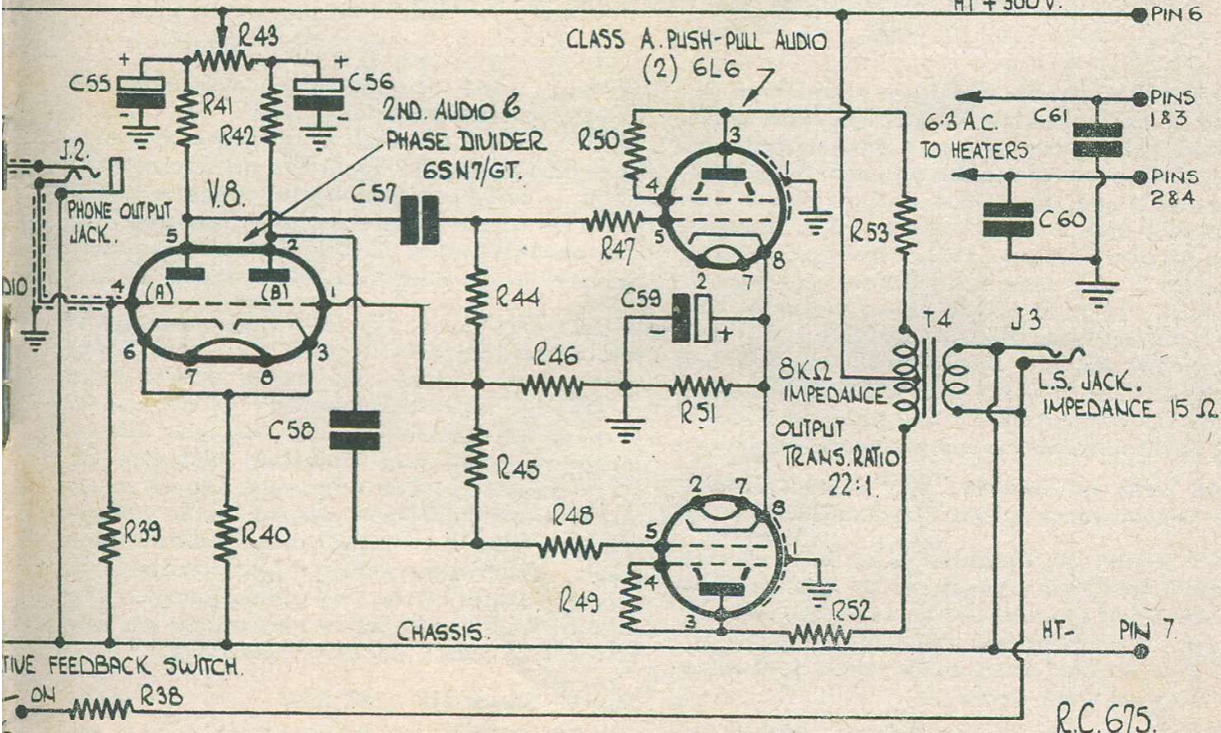

Frequency Coverage of the Receiver

Range 1	18.5—7.5 Mcs (16.2—40 metres)
2	7.5—3.0 Mcs (40—100 metres)
3	1,500—600 kcs (200—500 metres)
4	500—200 kcs (600—1,500 metres)
5	200—75 kcs (1,500—4,000 metres)

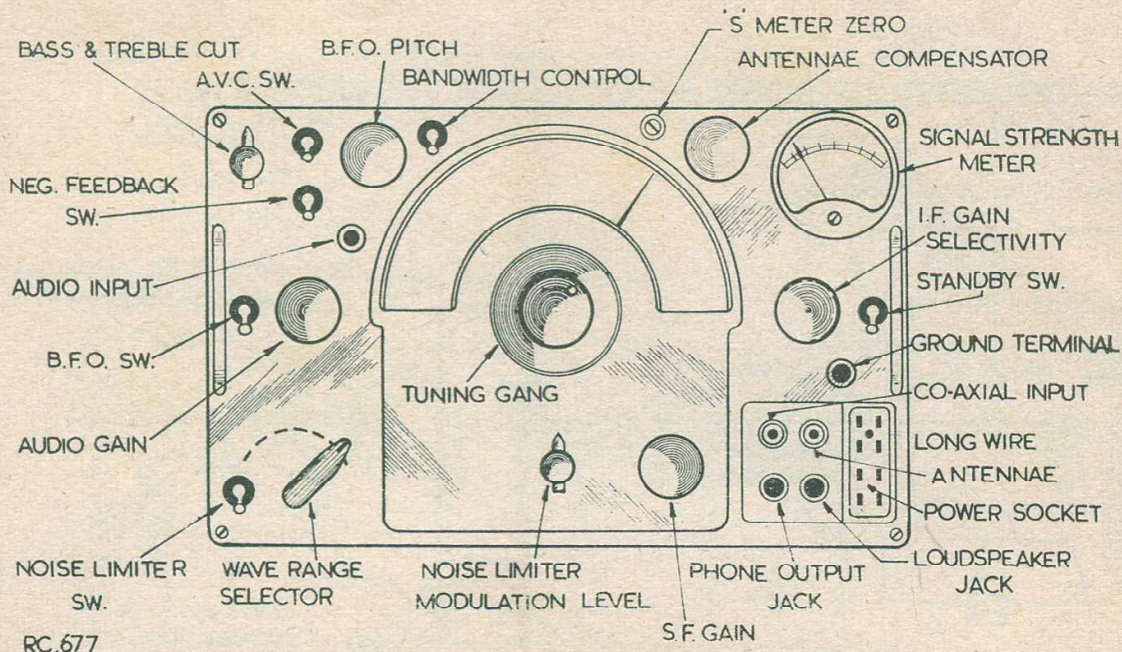

Showing revised layout of Control Panel (not to scale)

on top of the chassis and their connections are made to pins appearing through apertures in the chassis. The group of three pins nearest the edge of the receiver are the primary connections for range 4 and the nearest of these pins is disconnected from its earthing tag. The opposite three pins are connected to the secondary winding of range 4 and, here, the blue covered wire is removed. In each of the above instances, the corresponding pins for the remaining two LF ranges are similarly treated. No changes are required to the three HF coils which are mounted within the compartment. The alterations necessary to the remaining switch wafer are as follows :

Upper series of contacts : Key contact nearest inter-compartment screen is grounded.

Lower series of contacts : The key contact nearest screen is connected to the antenna capacitor and provides the input for the two HF ranges. Remaining key contact, on the reverse side of wafer, and contacts for ranges 3, 4 and 5 are removed from circuit.

The grid circuit filter unit in the SFA input (mounted on top of the LF range coils) is dispensed with although one component, the 160pF capacitor, is retained to maintain the tracking characteristics and is mounted under the chassis near the appropriate switch wafer. The lead from it to the tube grid is screened. However, the anode circuit filter, mounted in the middle of the larger compartment remains unaltered.

Two controls are provided for this stage. One is the variable antenna compensator C4 located on the front panel and it allows one to trim the

SF stage when using different antennae and also to correct the tracking errors. The other, a variable resistor R1, controls the gain of the stage by regulating the HT applied to the screen of the EF39—a most essential feature when receiving powerful signals to prevent the 'blocking' (or cross modulation) of the first detector (frequency changer) which might otherwise occur.

The triode-hexode type of frequency-changer is retained as the performance is quite satisfactory up to about 14 Mcs. The use of the converter is desirable above this frequency in any case in view of the double frequency-changing (better image rejection) and additional high-gain SF stage employed. The frequency-changer screen and local oscillator anode are fed by the voltage-regulator tube to assist the general stability of the stage. The switch wafers remain unaltered in this, the larger of the two compartments. The biasing and decoupling arrangements are new and will, of course, necessitate rewiring.

The IF Stages (IF—560 Kcs)

The first IF (6SG7) tube is located next to the main coil unit and in line with the SFA and frequency-changer tubes. It is with this stage that the first important departure from the original occurs, for this tube is made regenerative to give a degree of variable selectivity together with its single signal reception properties. This simple device gives very useful results by rejecting, in many cases, unwanted signals which may break through the first tuned circuits. Better results still may be obtained with a crystal filter circuit but the method used saves the considerable

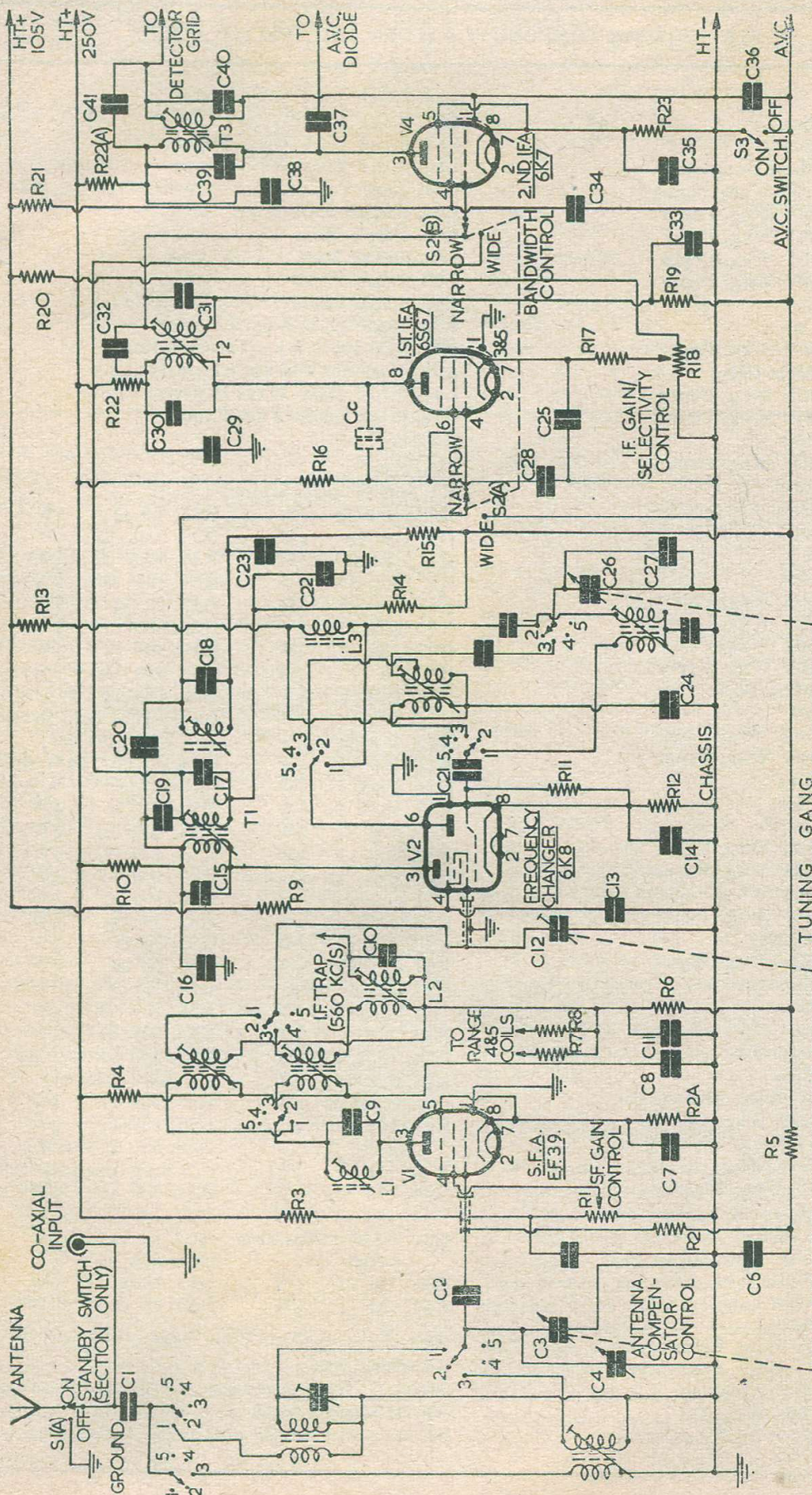


Fig. 2a. Circuit of the SFA, Frequency Changer and two IF Stages. Note: Only coils for ranges 1 and 3 are shown. Coils for ranges 4 and 5 are similar in design to those of range 3, and range 2 coils are similar to those for range 1. Certain switch sections, used to shunt out idle coils, are also omitted in the interests of simplicity, no modifications to the original being necessary in these sections.

RC676

TABLE SHOWING COMPONENT VALUES AND SPECIFICATIONS

Capacitors

C1, 200pF Mica
 C2, 160pF Mica
 C3, Section Main Gang
 C4, 20pF Variable air-spaced
 C5, 0.5μF 350V Wkg, Paper
 C6, 0.1μF 250V Wkg, Paper
 C7, 0.1μF 250V Wkg, Paper
 C8, 0.1μF 350V Wkg, Paper
 C9, 160pF, Mica
 C10, 0.002μF Mica
 C11, 0.1μF 250V Wkg, Paper
 C12, Section Main Gang
 C13, 0.1μF 350V Wkg, Paper
 C14, 0.1μF 250V Wkg, Paper
 C15, 300pF Mica
 C16, 0.1μF 350V Wkg, Paper
 C17, 300pF Mica
 C18, 300pF Mica
 C19, 8pF Mica
 C20, 2pF Mica
 C21, 200pF Mica
 C22, 0.1μF 250V Wkg, Paper
 C23, 0.1μF 250V Wkg, Paper
 C24, 0.1μF 350V Wkg, Paper
 C25, 0.1μF 250V Wkg, Paper
 C26, Section Main Gang
 C27, 15pF Mica
 C28, 0.1μF 350V Wkg, Paper
 C29, 0.1μF 350V Wkg, Paper
 C30, 300pF Mica
 C31, 300pF Mica
 C32, 2pF Mica
 C33, 0.1μF 250V Wkg, Paper
 C34, 0.1μF 350V Wkg, Paper
 C35, 0.1μF 250V Wkg, Paper
 C36, 0.1μF 250V Wkg, Paper
 C37, 50pF Ceramic
 C38, 0.1μF 350V Wkg, Paper
 C39, 600pF Mica
 C40, 300pF Mica
 C41, 4pF Mica
 C42, 0.5μF 350V Wkg
 C43, 250pF Mica
 C44, 4μF 500V Wkg, Electrolytic
 C45, 0.1μF 350V Wkg, Oil
 C46, 25μF 25V Wkg, Electrolytic
 C47, 0.1μF 350V Wkg, Oil
 C48, 8μF 500V Wkg, Electrolytic
 C49, 400pF Mica
 C50, 0.002μF Mica
 C51, 0.1μF 350V Wkg, Oil
 C52, 0.25μF 350V Wkg, Oil
 C53, 0.001μF Mica
 C54, 0.01μF Mica
 C55, 8μF 500V Wkg, Electrolytic
 C56, 8μF 500V Wkg, Electrolytic
 C57, 0.1μF 350V Wkg, Oil
 C58, 0.1μF 350V Wkg, Oil
 C59, 50μF 50V Wkg, Electrolytic

C60, 0.5μF 250V Wkg, Paper
 C61, 0.5μF 250V Wkg, Paper
 C62, 0.1μF 250V Wkg, Paper
 C63, 0.1μF 250V Wkg, Paper
 C64, 75pF Variable Air-spaced
 C65, 0.01μF 350V Wkg
 C66, 100pF Mica
 C67, 300pF Mica
 C68, 7.5μF Paper
 C69, 7.5μF Paper
 C70, 16μF 500V Wkg, Electrolytic
 C71, 8μF 500V Wkg, Electrolytic
 C72, 16μF 500V Wkg, Electrolytic
 C73, 0.1μF 500V Wkg, Paper
 C74, 0.1μF 500V Wkg, Paper
 Cc, See Text

Resistors

R1, 50k Ω variable wire	
R2A, 220 Ω $\frac{1}{2}$ W	R34, 30 Ω $\frac{1}{2}$ W
R3, 27k Ω $\frac{1}{2}$ W	R35, 6.5k Ω $\frac{1}{2}$ W
R4, 2.2k Ω $\frac{1}{2}$ W	R36, 100k Ω $\frac{1}{2}$ W
R5, 100k Ω $\frac{1}{2}$ W	R37, 18k Ω $\frac{1}{2}$ W
R6, 150k Ω $\frac{1}{2}$ W	R38, 2k Ω $\frac{1}{2}$ W
R7, 220k Ω $\frac{1}{2}$ W	R39, 560k Ω $\frac{1}{2}$ W
R8, 220k Ω $\frac{1}{2}$ W	R40, 900 Ω $\frac{1}{2}$ W
R9, 470 Ω $\frac{1}{2}$ W	R41, 42k Ω 1W ± 10%
R10, 2.2k Ω $\frac{1}{2}$ W	R42, 42k Ω 1W ± 10%
R11, 47k Ω $\frac{1}{2}$ W	R43, 10k Ω variable
R12, 270 Ω $\frac{1}{2}$ W	wire (pre-set)
R13, 470 Ω $\frac{1}{2}$ W	R44, 0.25M Ω $\frac{1}{2}$ W ± 5%
R14, 100k Ω $\frac{1}{2}$ W	R45, 0.25M Ω $\frac{1}{2}$ W ± 5%
R15, 100k Ω $\frac{1}{2}$ W	R46, 0.22M Ω $\frac{1}{2}$ W
R16, 47k Ω $\frac{1}{2}$ W	R47, 4.7k Ω $\frac{1}{2}$ W
R17, 150 Ω $\frac{1}{2}$ W	R48, 4.7k Ω $\frac{1}{2}$ W
R18, 2.5k Ω variable	R49, 100 Ω $\frac{1}{2}$ W
wire	R50, 100 Ω $\frac{1}{2}$ W
R19, 100k Ω $\frac{1}{2}$ W	R51, 375 Ω 5W
R20, 47k Ω $\frac{1}{2}$ W	R52, 50 Ω $\frac{1}{2}$ W
R21, 470 Ω $\frac{1}{2}$ W	R53, 50 Ω $\frac{1}{2}$ W
R22 and R22(A),	R54, 7k Ω 10W
2.2k Ω $\frac{1}{2}$ W	R55, 10k Ω $\frac{1}{2}$ W
R23, 270 Ω $\frac{1}{2}$ W	R56, 50k Ω 1W
R24, 150k Ω $\frac{1}{2}$ W	R57, 250 Ω variable
R25, 22k Ω $\frac{1}{2}$ W	wire (pre-set)
R26, 220k Ω $\frac{1}{2}$ W	R58, 600 Ω $\frac{1}{2}$ W
R27, 10k Ω variable	R59, 240 Ω $\frac{1}{2}$ W
wire	R60, 550 Ω variable
R28, 40k Ω $\frac{1}{2}$ W	wire (pre-set)
R29, 47k Ω $\frac{1}{2}$ W	R61, 400 Ω $\frac{1}{2}$ W
R30, 30k Ω $\frac{1}{2}$ W	R62, 1M Ω $\frac{1}{2}$ W
R31, 0.5M Ω variable	R63, 1k Ω $\frac{1}{2}$ W
carbon	R64, 50k Ω $\frac{1}{2}$ W
R32, 1M Ω $\frac{1}{2}$ W	R65, 100k Ω $\frac{1}{2}$ W
R33, 1M Ω $\frac{1}{2}$ W	R66, 1k Ω 10W

Note :Tolerances ± 20% unless otherwise stated.

Switches

S1(A), S1(B), Double pole, Double throw, Toggle.
 S2(A), S2(B), Double pole, Double throw, Toggle.
 S3, Single pole, Single throw, Toggle.

S4(A), S4(B), Double pole, Double throw, Toggle.
 S5(A), S5(B), 2-pole, 6-way, Rotary.
 S6, Single pole, Single throw, Toggle.
 S7, Single pole, Single throw, Toggle.
 S8(A), S8(B), Double pole, Double throw, Toggle.
 S9(A), S9(B), Double pole, Double throw, Toggle.

Inductances

L1, L2, L3, As original.
 L4, RF Choke, effective at 560 kcs 17.0mH Eddystone.
 L5, As original, or 560 kcs coil tapped one-third from grounded end.
 L6, L7, 3,400 μ H, DC resistance < 20 Ω .
 L8, LF Choke, 13H at 100mA (DC resistance 200 Ω).
 L9, LF Choke, 20H at 100mA (DC resistance 470 Ω).

Transformers

T1, IF Coil modified as per text.
 T2, T3, IF Coil as original.
 T4, Output transformer, ratio 22:1 (Wharfedale W.12).
 T5, Mains transformer, 350-0-350V 200mA, 6.3V CT 5A 5V 3A (Varley EP60)
 T6, Heater circuit, booster transformer—if necessary 6V 1.5A

Miscellaneous

M, Moving-coil meter, 0-1mA FSD, 2 $\frac{1}{2}$ " flush mounting, 75 Ω .
 J1, J2, J3, Jacks.

Note : Specifications and/or types of component used in author's receiver are shown in brackets.

cost of the crystals and gets over the mechanical difficulty of finding space and mounting satisfactorily—not to mention the difficulty of obtaining suitable 560 kcs crystals.

However, this stage is only necessary when high selectivity and sensitivity are required; this is not normally the case when receiving strong signals for, under such circumstances, this stage of the receiver serves only to suppress the sidebands and introduce distortion which would seriously impair the high-quality performance of which the audio stages are capable of producing. In view of this fact, a switch has been introduced to cut the first IF amplifier out of circuit in order to offer a comparatively wide bandwidth when required. It will be observed from the circuit diagram that an additional 560 kcs coil has been introduced into L3 in order to feed V4 direct when the selectivity switch is in the "wide" position. This coil is mounted between the two existing coils in L3 and should be of a similar type. IF transformers for 560 kcs can sometimes be obtained on the surplus market but if the constructor has difficulty in obtaining this item he is best advised to pile wind a coil on a similar former using the data supplied by an Abac chart or, alternatively, by adapting a standard 465 kcs inductance removing turns by trial and error. All leads to and from the selectivity should be carefully screened and earthed—preferably at each end. The stage is made regenerative by soldering a short length of wire to the plate terminal of the tube socket and running it near the grid terminal. The capacitance, so introduced, is indicated by Cc in the circuit diagram. Regeneration is controlled by reducing the gain of the tube and R18 a variable cathode bias control services this function. The nearer the tube is operated to the point of oscillation, the greater will be the selectivity. Bias voltage is obtained from the voltage regulated line to ensure smooth and constant regeneration characteristics. Incidentally, without the capacitance Cc, the amplifier should be perfectly stable and show no tendency to oscillate at full gain.

The second IF stage uses a 6K7, selected because high gain is not necessary at this point and, as indicated above, functions as the sole IF amplifier when the selectivity switch is in the "Wide" position. Screen voltage is supplied from the voltage regulator. The centre tap on the primary of the last IF transformer is not required and the lead may be removed. It will be noted that in this, and the previous stages, the biasing arrangements of the original circuit have been dispensed with and individual cathode biasing is used; thus the receiver chassis is no longer 'live' in respect to the power pack chassis.

Detector

An infinite impedance detector (6C5) was chosen because it combines the high signal handling capabilities of the diode detector with low distortion (good linearity) and, like the plate detector, does not load the circuit to which it is connected. An RF choke is included in the cathode lead to suppress any RF which might otherwise appear in the output—this component should, of course, be effective at 560 kcs. The tube base is located alongside the third IF transformer in order to keep the input leads as short as possible.

Beat Frequency Oscillator

As already described, the BFO (6C5) is mounted on a separate chassis which provides increased stability and screening. Coupling to the second detector is by the small capacitance formed by running an insulated wire from the grid of the BFO close to the detector grid prong on the tube socket. Very little coupling is needed for satisfactory operation; the remainder of the coupling lead must be screened. The oscillator coil may be the original component (tuned to 280 kcs) or a 560 kcs IF coil and should be mounted nearest the front panel with the tube immediately to the rear.

(To be concluded in next issue)

Rebuilding an Ex-RAF RECEIVER, Type 1155

By J. COOK

Noise-Limiter

Before the signal is fed from the detector to the first of the audio stages, it passes through a series type noise-limiter (6H6) which facility is provided by one section of the double-diode. The tube is arranged under the chassis with the holder near the wave-range switch panel bushing—it is essential for this tube to be of the small metal type to fit in the space available. This device 'chops' noise peaks by means of biasing the diode which becomes non-conducting above a pre-determined signal level. The point at which cut-off occurs is selected by adjustment of the control potentiometer R27 and this is adjusted on a signal until distortion commences. The control is then retarded slightly to clear the signal of distortion and will then limit noise with a higher amplitude than that of the signal. Varying signal strengths will necessitate a readjustment of this control, but AVC action will assist under such circumstances. Care should be taken with

bias is applied to the SFA, Frequency-changer and first IF stages. The majority of the AVC and noise-limiter components may be located on the tag board underneath the wave-range switch bushing.

'S' Meter Amplifier

The AVC coupling capacitor C37 also provides the necessary voltages to the EBC33 tube which is used to deflect the signal strength 'S' meter. This tube is mounted horizontally on a bracket attached to the guard rail above the output transformer which, provided the bracket is made of some rigid material, provides a substantial mounting. The rear bracket of the former system switch is suitable for this purpose. A separate tube has been used here primarily to operate the 'S' meter irrespective of whether the AVC is in use or not. Usually the 'S' meter is included in the plate circuit of one of the AVC controlled stages with the limitation that it becomes inoperative when the AVC is switched 'Off.' A

PRESENTING THE CONCLUDING INSTALMENT OF THE WINNING ENTRY IN OUR RECENT RECEIVER CONTEST


the screening of all wires of any considerable length carrying the audio signal from this stage up to the final amplifiers. A switch is provided to cut the limiter out of circuit as it does incur a slight loss of audio output besides complicating operation whilst tuning.

Automatic Volume Control

The remaining half of the 6H6 double-diode is used to supply the AVC voltages. The diode plate is fed from the second IF plate through a small coupling capacitor C37. The switch S3 cuts the AVC out of use by grounding the rectifier output. The time constant is arranged to give optimum results on slow fading although this part of the circuit may well be expanded by the use of a rotary switch offering a variety of time constants, if it is so desired. AVC control is not delayed in view of the fact that it may be switched off for the reception of weak signals. Control

normal 0.1 milliammeter (i.e., meter scale reading left to right) in a 'Bridge' circuit is arranged so that the meter reading and signal increase together. R60 should be adjusted for zero setting of the meter whilst R57 controls the meter sensitivity. It will be found that on strong signals the meter will be overloaded but, in fact, when this condition occurs it will be found that the frequency-changer is being over-loaded also (distortion will be apparent) so that if the gain of the receiver is adjusted such that the 'S' meter does not exceed its normal maximum deflection, protection against maladjustment will thus be afforded. Calibration of the meter is difficult as there does not appear to be any fixed standard for 'S' markings but, at all events, calibration will hold good only whilst the receiver is operated at the same frequency and conditions as obtained at the initial calibration. E.g., use of a converter

Fig. 4. Circuit of 1st AF amplifier using a 6SJ7 instead of a 6C5, with alternative method of using negative feedback.

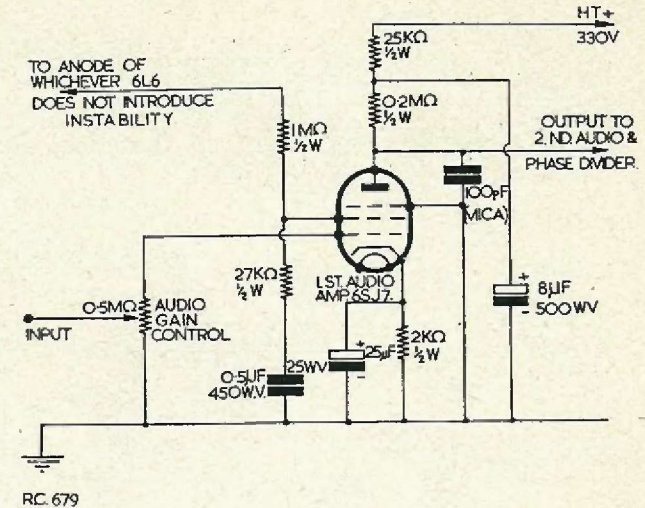

ahead of the receiver will result in higher gain and higher 'S' meter readings in consequence. Nevertheless, a signal strength meter is extremely useful for comparison of signal strengths and also for accurate tuning and alignment.

First Audio Amplifier

From the noise-limiter the audio signal is fed into the first stage of audio amplification (6C5) which is of moderate gain in view of the relatively high output from the detector. A small degree of negative feedback from the output transformer is introduced into the cathode circuit but this arrangement is controlled by a switch on the control panel as the full audio output is restricted by its use and this may not always be desirable. A jack is included in the input to enable the TRF units or pick-up to be fed into the audio amplifier. It is advisable to use a tube here that is very good mechanically if a noiseless background is to be obtained. Should higher gain be required, a 6SJ7 (pentode) may be used, instead of the 6C5, in the manner shown at Fig. 4. In this circuit an alternative method of applying negative feedback is adopted (without switching) and the coupling to the output transformer is dispensed with. Another jack, for feeding a pair of high resistance headphones, is included in the plate circuit together with a tone control giving four degrees of bass cut and two degrees of treble cut.

Second Audio and Phase Inverter Stage

A 6SN7/GT double-triode is used in the second audio and 'Floating Paraphase' phase inverter stage to drive the two final push-pull 6L6's. V8(a) functions as a normal amplifier whilst V8(b) provides the necessary phase inversion. Little additional gain is obtained from using a double tube but the advantage is that only one of the output tubes has to be driven by each section—thus it is easier to obtain the necessary

50 volts, peak to peak, required by the final pair of tubes, i.e., an input of 25 volts to each grid. Further, this circuit is substantially self-balancing*, obviating the necessity of special adjustment. The variable resistor in the anode circuits has been included in order to match the anode load resistors accurately and at the same time provide a small amount of decoupling.

Push-Pull Output Stages

The two output tubes are 6L6 beam tetrodes strapped as triodes and provide a maximum output of 6.5 watts as operated here in Class 'A.' Tubes must be of the metal or 'GT' variety in view of the space limitations. Output from the transformer, which should be a high grade component, is fed via the jack J3 to a filter circuit (housed in one of the speaker cabinets) which, with a cross-over frequency of about 1,000 cycles feeds two speakers with separate high and low frequency outputs. The position of these two speakers in relation to the listener has some importance in the resultant balance also they should be mounted in cabinets or on baffles of adequate dimensions. In the author's case, two 9" 'Gramian' units are used as they provide a wide and moderately level frequency response with large power handling abilities (7 watts apiece) for a reasonable outlay.

*For explanation, see "Radio Designer's Handbook" by F. Langford Smith.

The Power Supply

The power supply is housed in a separate unit. This is necessary because there is no possible room for these bulky components on the receiver chassis which is now full to overflowing! Not only this, but it is desirable to keep the transformers and chokes away from the main receiver as these components are always a potential source of inductive hum; also extra heat is generated by

H.T. CONSUMPTION			L.T. CONSUMPTION		
UNITS IN USE	MIN	MAX	VOLTAGE	UNITS IN USE	CURRENT
AMPLIFIER PLUS ADAPTER	—	150 ma	5.0V	V14	3 AMPS
RX ONLY	135 ma	145 ma	6.3V	ALL	6.63 AMPS
RX PLUS ADAPTER	140 ma	150 ma	6.3V	RX PLUS ADAPTER	5.6 AMPS
RX PLUS ADAPTER PLUS CONVERTER	165 ma	—	6.3V	RX PLUS CONVERTER	6.09 AMPS
RX PLUS CONVERTER	150 ma	160 ma			

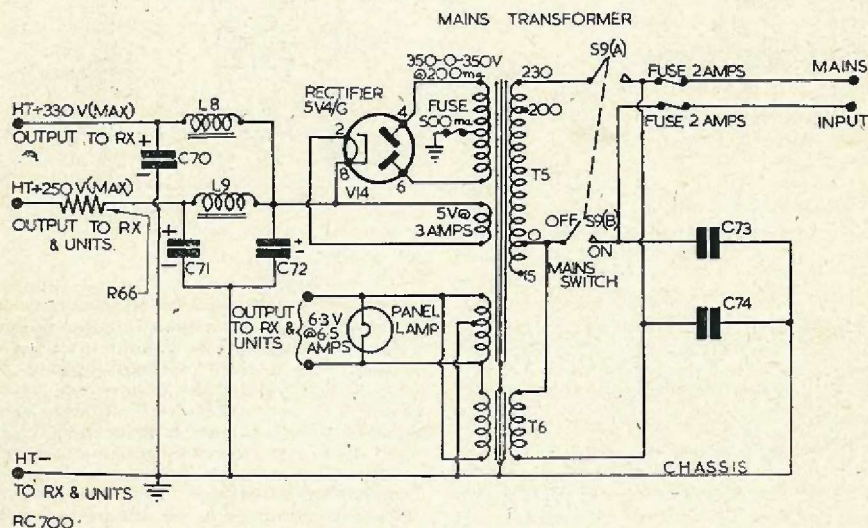


Fig. 2(c). Circuit of the Power Supply Unit.

the rectifier and dropping resistors which, again, is best isolated from the receiver.

This unit is required to supply a total of 21 tubes (excluding neon stabiliser) and, in consequence, the parts are of substantial proportions. Outputs are arranged to supply 250 volts and 330 volts to the RF and AF stages respectively. Separate smoothing chokes are used for each voltage in order that lower (current) rated chokes may be used. If chokes with differing DC resistance characteristics from those specified are used, appropriate adjustments to the dropping resistor R66 and a further dropping resistor in the output from the rectifier may be necessary to obtain approximately the above-mentioned outputs. Similar adjustments may be necessary if an alternative type of rectifier is used.

Smoothing is adequate, and if screening and layout has been given due care and attention in the receiver and amplifier, there should be negligible hum in the output.

Little need be said of construction because Fig. 5 shows the layout clearly, whilst exact dimensions and wiring are of little importance

except that, once again, it must be borne in mind that the portion of the multi-cable carrying the 6.3 volts heater supply must be capable of passing the 5 amps current without any drop in voltage. The cable is terminated at the receiver end by an 8-pin 'Jones' type plug which fits into the remaining socket on the receiver chassis which now carries the supply voltages. In view of the heavy heater requirements when all the associated equipment is in use, an additional booster transformer is connected in parallel across the 6.3 volt section of the main transformer. It is important that the additional transformer is connected in the correct phase relationship—when connected in anti-phase this condition will be recognised by rapid heating of the transformer. Of course, if a transformer is obtained which is capable of supplying the requisite 6 to 7 amps the booster transformer will not be necessary—unfortunately few manufacturers seem to cater for such relatively large heater demands in the 200/250 mA class of transformer. The voltage regulator tube is properly part of the power pack but it is, for convenience, located underneath the main

receiver chassis next to and in line with the 6H6 rectifier and the associated load resistor R54 has been placed on a tag strip mounted on the coil pack near the side of the case for ventilation.


Operation

The first step in putting the receiver into operation, assuming all is well, will be to align the IF stages as it will be found that rewiring will have altered the alignment considerably. Note that it is necessary to align the two secondary winding in their respective "Narrow" and "Wide" bandwidth positions. The IF trap L2 is adjusted so that instability does not occur when the receiver is operated near the IF frequency. Alignment of the SF and Frequency-changer stages should not be necessary if this was satisfactory before conversion but it will be found necessary to decrease the capacity and/or inductance of the SFA grid circuit coils to allow for the inclusion of the antenna compensator control.

The Ultra High-Frequency Converter

The highest frequency covered by the converted receiver is 17 Mcs so that a converter unit is necessary if it is desired to extend the frequency range.

The converter used by the author is basically the 'Eddystone' UHF 5-10 metre converter, described in 'Eddystone' Short-Wave Manual No. 5. HT stabilisation (VR105/30) has been incorporated to mitigate frequency drift which is an especial consideration when used in conjunction with the narrow bandwidth of the main receiver. A complete set of self-supporting plug-in coils can be constructed from 14 gauge wire to cover 60 to 30 Mcs, and as the converter is capable of an

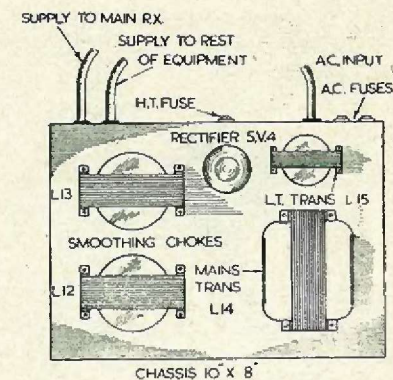

RC 698

Fig. 5. Layout (not to scale) of the Power Pack.

exceptionally fine performance on the lower frequencies as well, coils may also be constructed to cover down to, for example, 14 Mcs. Formers will be necessary for these lower frequencies and polystyrene tubing will be found to be a convenient material for this purpose, using 6 BA brass rod for pins—the ends being turned down to the requisite diameter to fit the coil base sockets. The main receiver should be tuned to the highest frequency on range 3 for use with this unit, i.e., approx. 1,550 kcs. It is interesting to note that this converter may be used very effectively as a two stage pre-amplifier when the SFA/Mixer gang is tuned to the desired frequency and the local oscillator coil is removed.

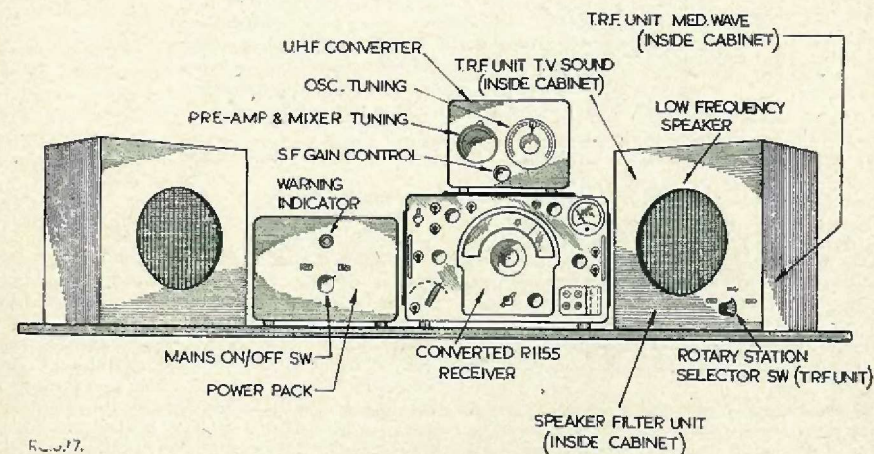


Fig. 7. General view of the equipment described.

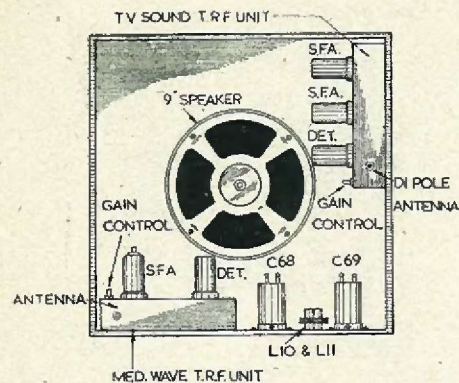


Fig. 6. Loudspeaker Unit, housing the Filter and TRF units.

Medium Wave TRF Unit

A need for a unit of this type was felt because, with a superhet, it is difficult to obtain a band-pass sufficient to cover the 16 kcs radiated without attenuation of the side-bands due to the multiplicity of the circuits in the superhet. Two tubes are used—the first being a conventional signal frequency amplifier (6K7) incorporating a gain control to counteract 'blocking' of the detector

when receiving strong signals. A second SF stage may be necessary in areas of low field strength or to improve adjacent channel rejection in difficult locations. In either case, efficient coils having a high 'Q' are desirable in this and the detector stage.

The detector is of the infinite impedance (negative-feedback) type and the circuit may be similar to that employed in the main receiver.

Station selection is effected by a rotary switch which selects alternative pre-set capacitors (high-permeability type); one position on this switch breaks the HT and antenna inputs in order that the main receiver may be operated.

Television Sound TRF Unit

For reasons similar to those stated above, a TRF receiver also offers the finest results when receiving the sound accompaniment to the television transmissions. Again an infinite impedance detector has been used, this time in conjunction with two stages of SFA using EF50's in a circuit similar to the "Wireless World" or "Electronic Engineering" television sound sections.

The two of these TRF units together with the loud-speaker dividing network are housed in one of the speaker cabinets, thus making for a neat installation as illustrated at Fig. 6.

When operating either of the TRF units and only using the amplifier portion of the main receiver, it is advisable to switch the 'Standby' switch (S1) to the 'Off' position for best quality as well as muting the RF stages.

SURPLUS RADIO EQUIPMENT

described by B. Carter

In this series of articles it is intended to describe units that have (a) immediate application, after some modification perhaps, in the amateur world, and (b) to list the contents of those units that can best become sources of valuable components. This month's unit with very little modification may be of use to many amateurs as it is purchased.


CONTROL UNIT TYPE 409 (10 LB/6009)

THE name of this unit belies its true value to the amateur, the main attraction being the power unit which feeds the control valves. The removal of the control section leaves ample room for modifications, for example as a stabilised and regulated power unit, or as an output stage/power unit of the kind used for such receivers as the R1155.

The chassis and front panel are of heavy gauge steel welded together and the cover is similarly strong with louvres on all vertical surfaces. Anti-rattle clips are provided inside the front panel, making a very sturdy case 8½" long x

7½" high x 8½" deep.

The power unit is formed around a full-wave rectifier valve in the usual manner, employing a choke L2 and capacitor C9 for smoothing. The transformer HT secondary is labelled "300V 40mA" but it is thought that this is a very conservative estimate of its current rating, having due regard to the core size. The mains input is by way of the "W" plug, 230 volt 50 cycles between pins 1 and 4 or 80 volts 1,000 cycles between pins 1 and 2. The colour code shown may not be universal and may differ from that used in units of a different order.

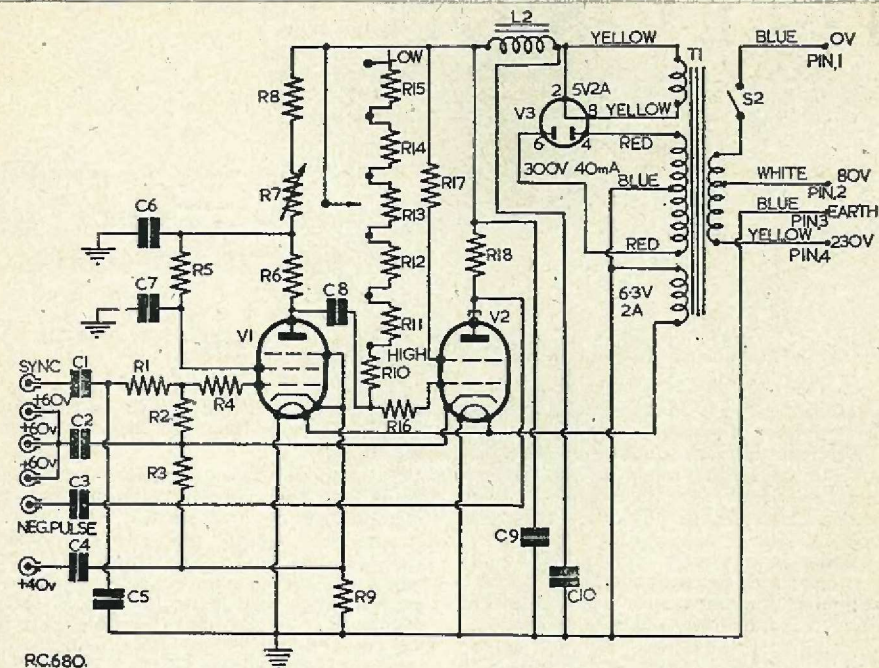

Circuit of the 409 Control Unit

CONTENTS LIST

R1, 4.7k ½W	C1, 30pF
R2, 75k high stability 10C/3622	C2, 0.1µF 350V
R3, 110 ½W	C3, 0.1µF 750V
R4, 220 ½W	C4, 0.1µF 750V
R5, 3.3k 2W	C5, 200pF
R6, 22k 5W	C6, 0.25µF 750V
R7, 5k potentiometer	C7, 0.25µF 750V
R8, 2.2k 1W	C8, 0.001µF mica
R9, 220 ½W	C9, 4.0µF 500V
R10, 3M ½W	C10, 8.0µF 500V
R11, 3.3M ½W	
R12, 1.3M ½W	
R13, 5.1M ½W	
R14, 2.4M ½W	
R15, 10M ½W	
R16, 220 ½W	
R17, 150 ½W	
R18, 330 ½W	

L1, Mains transformer

L2, Smoothing choke

S1, Single pole 6-way

S2, Single pole changeover

V1, VR91 (EF50) and holder

V2, 807 and holder

V3, 5Z4 and holder

One 4-pin plug type W198

Six single pole plugs 209

Carrying handle

Two groupboards

One 807 anode clip

(SIGNAL GENERATOR—contd. from page 244)

aligning a receiver by measuring the AVC voltage. Fig. 5 shows the circuit of a receiver which takes the AVC voltage from the anode of the last IF valve. This method of obtaining AVC is fairly common. It will be seen that the secondary of the IF transformer is not connected to the AVC circuit. However, this secondary may be adjusted by trimming it to give a decrease in AVC voltage. The reason for this is that the secondary tuned circuit acts as an absorption circuit, and, therefore, when accurately trimmed, it takes energy from the primary tuned circuit.

Whilst on this topic, the writer should like to state that if the constructor uses methods such as those shown above, then there is no reason why he should not make a really good job of aligning any receiver with which he has to deal. The actual procedure of aligning a modern receiver would require another series of articles to enable it to be adequately dealt with, and these would not readily fall in line with the subject-matter of the present contribution. Nevertheless, should readers be interested (and subject, of course, to the consent of the Editor), the writer is prepared to submit a series on the subject of modern receiver alignment, which may then be published in future issues of the "Radio Constructor." (What do readers think of this suggestion? —Ed.)

—To be concluded in next issue—