

Yaesu Musen FL2000B *revamped*

by N E Mattick VK2QF

"Blackwillow"

Hargraves NSW 2850

VK2QF has extended the life of his Yaesu FL 2000B Linear Amplifier with considerable ingenuity. However, constructors are warned that potentially lethal high voltages are employed in this amplifier and only experienced people should tackle this project

HAVING USED the old "FL2000B" amplifier on the ten metre band for 50Mhz dx liaison for some years in its original form until one day a heater failed and went across to the plate inside valve 1 giving a healthy spark and "all lights out" around the place. Needless to say some sort of service was due, especially since the HT had been shorted! Replacements for the 572B's were not considered due to their prohibitive price and poor survival. So some alternatives were seriously considered.

An initial "lash up" trial of two wartime 813 Pentodes was a failure due to low gain and excess plate stray capacitance placing the plate circuit beyond resonance on the ten and fifteen metre bands, (more on this topic later).

Not perturbed by this failure I continued to concentrate on a solution that proved to

be utterly successful in the end.

The parameters for the project were the following;

- Low IMD.
- Durability.
- A valve that would operate in any position.
- Low cost and recycling of otherwise discarded equipment.
- Minimal noise commensurate with adequate performance and heat removal,
- Parts must be on hand and or be made readily within a basic workshop,
- No physical changes to the appearance of the cabinet or front panel was allowed,

- High gain and equal performance across the range of bands that the amplifier was designed for, (in fact 10db of gain was realised meaning a Kenwood TS 570s as a driver will run a signal 3Db down on the legal limit Singlesideband signal),
- The basic design of cathode driven circuitry was to remain therefore any selected valve must either be a triode or more importantly be capable of triode (GROUNDED GRID CONNECTION), this was met by the chosen valve.

It is not intended to give a comprehensive description of the project as it is assumed that the builder will have sufficient experience to carry out the modifications to fruition. Furthermore this work only applies to the YAESU MUSEN FL2000B amplifier, just how this unit is different from later models eg. FL2100(B) is not known by the author, so should any builder decide

CATHODE TUNING CHART.

VSWR	INPUT INDUCTOR	INPUT C	OUTPUT C
1.4:1	Less one turn L202 = 15t > 80 mx	320 pf	150 pf
1.2:1	Less one turn L203 = 10t > 40 mx	400 pf	150 pf
1.2:1	Remove slug L204 = standard > 20 mx	250 pf	125 pf
1.2:1	Remove slug L205 = standard > 15 mx	110 pf	115 pf
1.2:1	Less one turn L206 = 4t > 10 mx	100 pf	140 pf

Note: 15 and 10 metre bands have variable capacitors to optimise loading. All fixed capacitors are SILVERED MICA types

Figure 1

TANK COIL CHART.

10 mx	4 turns from plate end
15 mx	8 turns from plate end
20 mx	12 turns from plate end
40 mx	20 turns from plate end
80 mx	29 turns from plate end

Figure 2

to modify one of these it remains their responsibility to adapt any differences in the basic design and circuit.

It is also necessary to highlight at the outset all inherent dangers when working with mains powered equipment let alone the HIGH TENSION voltages encountered in this amplifier as designed by YAESU MUSEN. This HIGH TENSION voltage is 2,400 volts which it needs to be made clear that contact with this is definitely lethal, so unless those who may attempt this work are experienced at working with these voltages it is recommended by the author that the work be done under the supervision of an experienced technician. *It is worth noting at this juncture that the author never "powered up", "worked on" or "modified" the amplifier without its full shields and covers fitted, during each phase of development, also the mains supply wiring is controlled by an "ELCD" or earth leakage circuit detector.*

To modify the amplifier the constructor will need the following;

- 1) 8352 / 4CX1000K tetrode in known good electrical condition, these seem to sell for approximately \$100 at hamfests. (It is possible that a similar result could be obtained with alternative valves, eg; 4CX1000A and 4CX1500B as they are electrically and mechanically similar).
- 2) Metal lathe.
- 3) 10 mm PTFE or perspex rod.
- 4) 90 mm stormwater pipe.
- 5) 65 mm alloy bar stock.
- 6) 8 x 220uF 400v or better miniature electrolytic capacitors
- 7) Air spaced capacitor 100pf to better than plate capacitor ratings of air gap.
- 8) 600pF to 1000pF 30Kv or better coupling capacitor.
- 9) 1 x 65ohm 20w resistor.
- 10) Sundry miscellaneous hardware, pcb,

relays and signal components.

- 11) Miniature blower to deliver a minimum 40cfm of air at 13mm Hg water column.

The simplicity of the project is the relinquishment of the need for the SK820 BREECHLOCK socket. These sockets are unprocurable and cost more than the valve at retail prices. Grid grounding and mounting are accomplished in one operation with both the Screen and Control grids being clamped together in a simple alloy split ring made from bar stock.

The three rings that compose this clamp are as follows;

- Screen ring, width 3mm,
- G1/G2 ring which is a snug fit into the lands between these two sets of radial terminals,
- Base ring of 3mm which is under the G1 terminals.

These are cut in half and bolted every 120° over the valve ceramic body. A thread is cut into the top or screen alloy ring and bolts which have three simple flat mounting lugs which reach out beyond the perimeter of the 70mm diameter hole that must be made in the wall of the former Grid compartment vertical chassis. As the tolerance of the valves varies it is up to the individual constructor to ensure that sufficient clearance is provided for thermal expansion of the valve when in use, therefore as a guide the author used 0.5mm

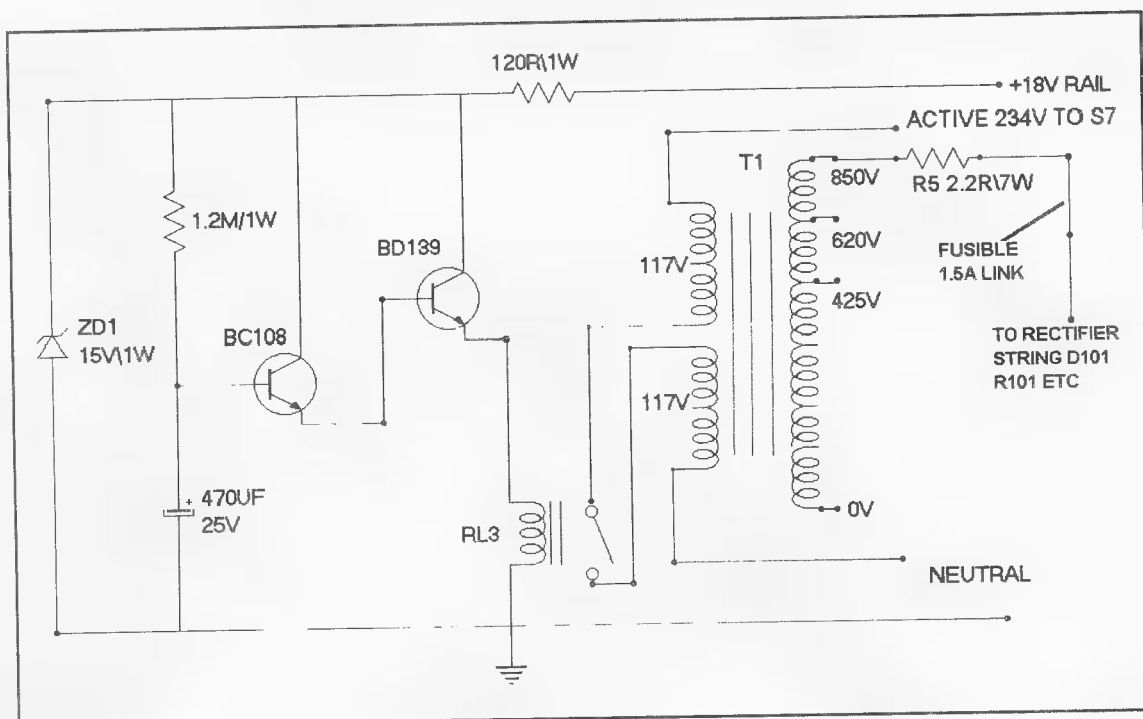


Figure 3. Timer Circuit

oversize for the alloy mounting rings based on the mean cylindrical measurement of the prototype 8352.

The 8352 is relocated to centralise the anode radiator in the plate compartment away from the original valve one mounting position.

The cathode compartment is largely unmodified except for;

L202 - L206 as per the chart Fig 1.

S2 is relocated away from the terminals of the 8352.

All unused holes in the compartment are fully sealed against RF and air leaks to maximise system performance, (silicon sealant is ideal for sealing the air leaks with bolts and washers for the smaller unused chassis holes).

The L2 bifilar choke is connected by leads directly soldered to the Heater and Heater Cathode terminals of the 8352, do not omit C205 as performance will be degraded.

A new rear panel is folded to suit the blower outlet and this will be quite up to the individual circumstances to determine its dimensions.

In the plate compartment some extensive development work must be done. To ensure adequate cooling for the 8352 and the fully mounted blower must be tested to ensure adequate back pressure drop across the plate radiator.

A simple chimney is fashioned from 90mm stormwater pipe, this product must

It is next essential to assure a 3 minute heater run up delay timer which after switch on delays by a predetermined time constant of τ/c as per Fig 3 (this circuit is powered by rectifying via D1 and filtering C1 the 13 volt winding in the original heater transformer T2). This timer controls RL3 which closes the circuit of T1 to the AC supply thus enabling HIGH TENSION voltages.

Also in Fig 5 is the DC control circuitry for the blower motor. Builders will have to adapt their own circumstances to suit in this area. The prototype blower was highly modified. Initially it's AC motor was removed and a substitute 3000 rpm high torque DC unit with bronze bearings was modified to take ball races, (most costly minor parts in the whole project!). This

This circuit also encompasses one more essential feature for protection of the 8352 and this is an after cool rundown timer Q3 / Q4. When the amplifier is turned off after heavy work it is possible to leave the 8352



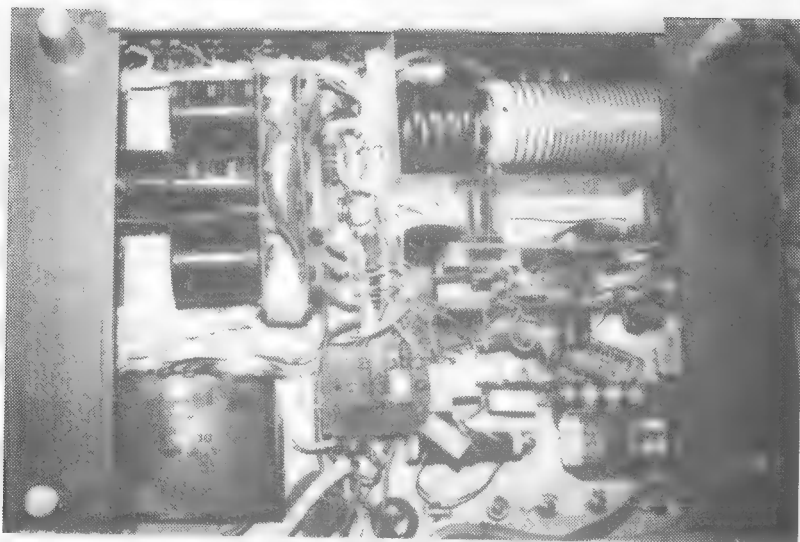


Photo 1: Power Supply and control systems

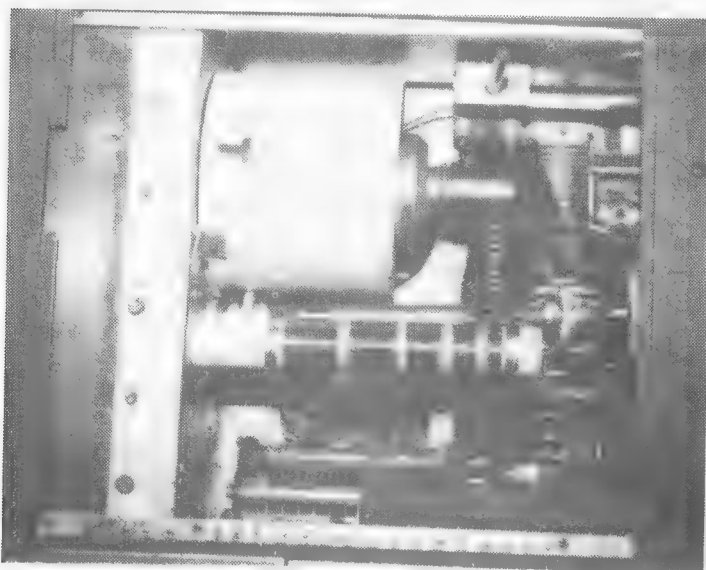


Photo 2. Output section — general layout

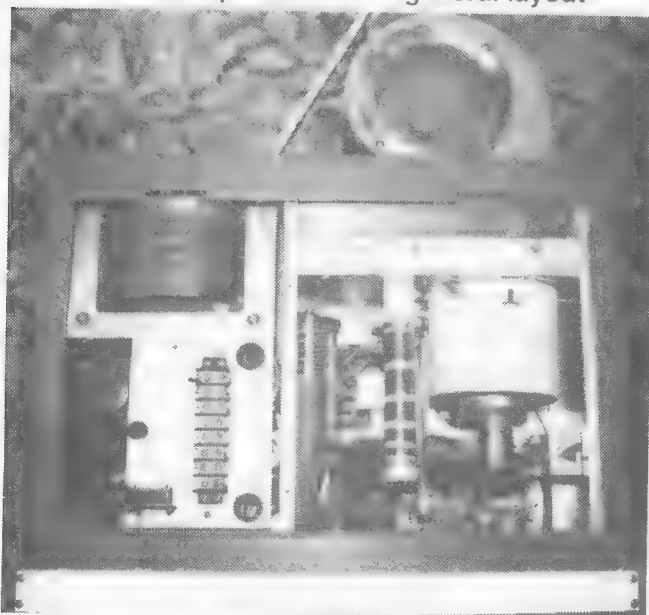


Photo 3. Amplifier — general layout (Blower)

overheated so rather than having to wait with the equipment whilst it aftercools for two minutes this is taken care of. The circuit senses HIGH TENSION voltage via a 10M ohm resistor at the cold end of the rectifier string (junction of R110 / R109) and continues powering the blower motor (via Q3, Q4, D2 and Q5) as the HT voltages bleed away.

Also in the power supply area attention must be given to the voltage doubler. The original capacitors must be replaced with suitable units to provide a total capacity of 25uF or better. By substituting 8 220uF miniature capacitors a total of 27.5uF was achieved. The need for this modification cannot be stressed too highly as performance will be severely degraded and IMD (intermodulation distortion) will increase if this area is not upgraded.

Other PSU changes are R4 the bias resistor (ref fig 5), is deleted and tapped in half to act as a surge limiting resistor. Two 0.1 ohm 5w resistors (ref fig 5 R3A & R3B) are placed in parallel with R3 thus doubling the plate meter scale to FSD of 1,200 mA. A 2.2 ohm 7 watt surge (ref fig 3 R5) limiting resistor is placed in the T1 HIGH TENSION tapping point, this goes to a fusible link as a safety precaution.

The hazard sheet from Varian specifies a tolerance for the heater voltage of six volts $\pm 5\%$. To ensure that it is correct remote leads were attached to the terminals of the 8352 and with air applied, the whole system was run so that the voltage could be read. T1 / T2 (both original units) are fully tapped out in their primary circuits to the 234v position giving them the best settings to run the 8352, even so the heater voltage from T2 is in excess so a 65 ohm 20 watt resistor (ref fig 4 R8) was needed in the primary circuit to correct this critical voltage.

Tuning and Testing

Once the constructor is totally confident all the modifications are complete a small amount of drive should be applied to the circuit and the alignment process begun. Setting of the input inductors is essential, this is best done with reference to the chart of modifications in Fig 1 and the Yaesu owners manual.

As a guide peak all tuning controls and measure the reflected power in the exciter line. Assess the necessary changes to be made either to the appropriate inductor or capacitors that are modified in the input circuit.

Since developing the amplifier it has had many hours of "ON AIR" use, mainly for semi break-in CW contesting where it has performed faultlessly. Whilst no "Lab" attempt has been made to assess the IMD

performance of the 8352 it appears using the equipment available that it is either the same to better than original.

One more point to bear in mind is that this amplifier had in it's original condition the ability to exceed the legal power limit for the Amateur service in Australia. The "revamp" described in this article also has the potential to exceed the power limit and constructors must ensure that the Regulations are complied with.

So there it is a faulty piece of equipment returned to vastly better use, now is the time to rebuild whilst the "SOLAR WINTER" is on and be prepared for bigger and better "DX" in cycle 23.

References

1: ARRL handbook for 1976, page 184 "A 160 Meter Amplifier".

ar

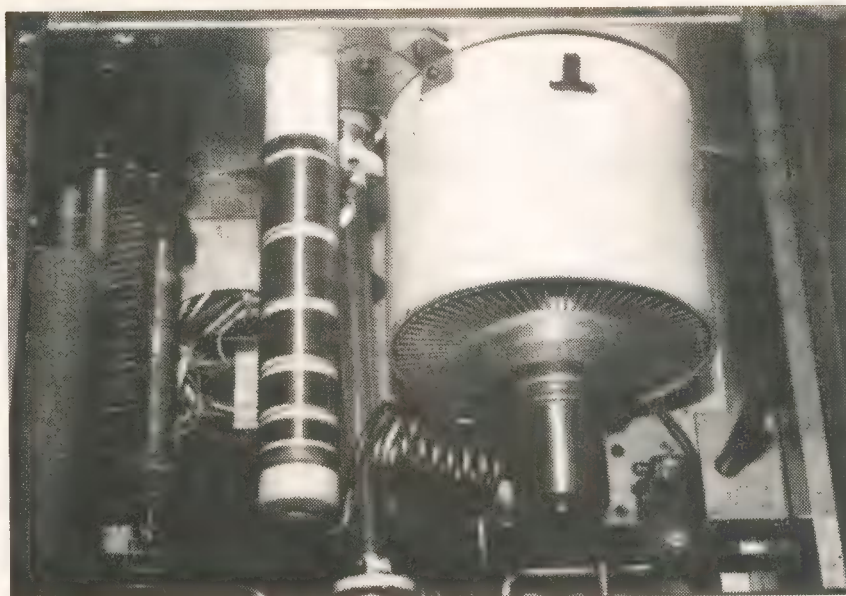


Photo 4. Output stage — tube detail

G. & C. COMMUNICATIONS

Graham Brennan VK3 KCS

19 Arleon Crescent, Cranbourne 3977

KENWOOD

GMEL Electrophone

uniden®

We specialise in Australia-wide mail order

(03) 5996 3298

e-mail: gccom@netspace.net.au

www.netspace.net.au/~gccom

Fax (03) 5995 0184

All major credit cards welcome

An active amateur offering professional service, advice and product.

Support
the Advertisers
who support

A Amateur
R Radio